

# Review of digital logic design

# Background


- Logic gates (AND, OR, NOT, XOR, etc.)
- Boolean algebra
- Truth tables
- Logic functions
- Logic function synthesis by
  - Sum of Products (SOP)
  - Product of Sums (POS)
  - K-maps
- Logic blocks (MUX, DEMUX)
- Sequential elements (Latch, Flip-flop)

# Logic gates



**AND**

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

 

**OR**

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1




**XOR**

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0




**NOT**

Input	Output
0	1
1	0

 


**NAND**

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

 

**NOR**


A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

 


**XNOR**

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1


# Generalized n-input logic gates

 


AND gates

 

NAND gates

 

OR gates

 

NOR gates

# Axioms of Boolean Algebra

- 1a.  $0 \cdot 0 = 0$
- 1b.  $1 + 1 = 1$
- 2a.  $1 \cdot 1 = 1$
- 2b.  $0 + 0 = 0$
- 3a.  $0 \cdot 1 = 1 \cdot 0 = 0$
- 3b.  $1 + 0 = 0 + 1 = 1$
- 4a. If  $x = 0$ , then  $x' = 1$
- 4b. If  $x = 1$ , then  $x' = 0$

# Boolean Algebra - Single Variable Theorems

- 5a.  $x \cdot 0 = 0$
- 5b.  $x + 1 = 1$
- 6a.  $x \cdot 1 = x$
- 6b.  $x + 0 = x$
- 7a.  $x \cdot x = x$
- 7b.  $x + x = x$
- 8a.  $x \cdot x' = 0$
- 8b.  $x + x' = 1$
- 9.  $(x')' = x$

## ● Boolean Algebra - Two Variable Properties

- 10a.  $x \cdot y = y \cdot x$  Commutative
- 10b.  $x + y = y + x$
- 11a.  $x \cdot (y \cdot z) = (x \cdot y) \cdot z$  Associative
- 11b.  $x + (y + z) = (x + y) + z$
- 12a.  $x \cdot (y + z) = x \cdot y + x \cdot z$  Distributive
- 12b.  $x + y \cdot z = (x + y) \cdot (x + z)$
- 13a.  $x + x \cdot y = x$  Absorption
- 13b.  $x \cdot (x + y) = x$
- 14a.  $x \cdot y + x \cdot y' = x$  Combining
- 14b.  $(x + y) \cdot (x + y') = x$

# Boolean Algebra - Two & Three Variable Properties

- 15a.  $(x \cdot y)' = x' + y'$  DeMorgan's theorem
- 15b.  $(x + y)' = x' \cdot y'$
- 16a.  $x + x' \cdot y = x + y$
- 16b.  $x \cdot (x + y) = x \cdot y$
- 17a.  $x \cdot y + y \cdot z + x' \cdot z = x \cdot y + x' \cdot z$  Consensus
- 17b.  $(x + y) \cdot (y + z) \cdot (x' + z) = (x + y) \cdot (x' + z)$



# Logic Function Synthesis - Three variable SOP & POS

- Function synthesis from truth table

Row number	$x_1$	$x_2$	$x_3$		Minterm	Maxterm
0	0	0	0		$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1		$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0		$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1		$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0		$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1		$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0		$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1		$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

# Logic Function Synthesis - 2/3/4 variable k-map

- Function synthesis using k-maps

$x_1$	$x_2$	
0	0	$m_0$
0	1	$m_1$
1	0	$m_2$
1	1	$m_3$

$x_1$	0	1
$x_2$		
0	$m_0$	$m_2$
1	$m_1$	$m_3$

$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
0	1	0	$m_2$
0	1	1	$m_3$
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$

$x_1 x_2$	00	01	11	10
$x_3$				
0	$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$

$x_1 x_2$	00	01	11	10
$x_3 x_4$				
00	$m_0$	$m_4$	$m_{12}$	$m_8$
01	$m_1$	$m_5$	$m_{13}$	$m_9$
11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

Diagram illustrating a 4-variable Karnaugh map (K-map) for variables  $x_1, x_2, x_3, x_4$ . The map is a 4x4 grid of cells, each labeled with a minterm  $m_i$ . The columns are labeled  $x_1 x_2$  (00, 01, 11, 10) and the rows are labeled  $x_3 x_4$  (00, 01, 11, 10). The map is partitioned into four 2x2 subgroups, each labeled with a variable:  $x_1$  (top row),  $x_2$  (bottom row),  $x_3$  (left column), and  $x_4$  (right column).

# Logic Function Synthesis - 2/3/4 variable k-map


Function synthesis using k-maps

1. No zeros allowed.
2. No diagonals.
3. Only power of 2 number of cells in each group. ( $2^0=1$ ,  $2^1=2$ ,  $2^2=4$ ,  $2^3=8$ , etc.)
4. Groups should be as large as possible.
5. Every 1 must be in at least one group.
6. Overlapping allowed.
7. Wrap around allowed.
8. Fewest number of groups possible.

Visit: <http://www.ee.surrey.ac.uk/Projects/Labview/minimisation/karrules.html>
 
# Multiplexer

- Multiple inputs, single output. Output is chosen by selector pin/s




Graphical symbol

$s$	$f$
0	$w_0$
1	$w_1$

Truth table

2x1 Multiplexer

 

Graphical symbol


$s_1$	$s_0$	$f$
0	0	$w_0$
0	1	$w_1$
1	0	$w_2$
1	1	$w_3$

Truth table


4x1 Multiplexer
 
# D Latch

- Level sensitive element
- *A positive level triggered D latch*
  - copies D to output Q, if Clock=1, else preserves the previous output
- *A negative level triggered D latch*
  - copies D to output Q, if Clock=0, else preserves the previous output



Graphical symbol

 


Clk	D	Q(t + 1)
0	x	Q(t)
1	0	0
1	1	1


Characteristic table
 
# D Latch

- Level sensitive element
- A **positive level triggered** D latch
  - copies D to output Q, if Clock=1, else preserves the previous output
- A **negative level triggered** D latch
  - copies D to output Q, if Clock=0, else preserves the previous output



Graphical symbol

 

Clk	D	Q(t + 1)
0	x	Q(t)
1	0	0
1	1	1




Characteristic table
   
# D Flip-flop

- Edge sensitive element






- A **positive edge triggered** D flip-flop
  - Sets  $Q=D$  at all positive edges (rising edges) of the clock, retains the old value of  $Q$  otherwise
- A **negative edge triggered** D flip-flop
  - Sets  $Q=D$  at all negative edges (falling edges) of the clock, retains the old value of  $Q$  otherwise



Graphical symbol
   
# Building D Flip-flops using D Latches




- By cascading a positive level triggered D latch and a negative level triggered D latch we can build a negative edge triggered D flip-flop




   
# Building D Flip-flops using D Latches

- By cascading a positive level triggered D latch and a negative level triggered D latch we can build a negative edge triggered D flip-flop



symbol of negative edge Flipflop

follow the Q<sub>m</sub>, clock\_bar signals to draw Q<sub>s</sub> ie, Q of the second latch

# Level triggered vs. Edge triggered

- In level triggered elements
  - output is affected by the clock levels (*high/low*)
- In edge triggered elements
  - output is affected by the clock edges (positive edge/negative edge) (rising edge/falling edge)

